

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING, KITSW


COURSE: U14EI 205 - BASIC ELECTRONICS ENGINEERING | ECE-I, Semester-II, 2015-16

ASSIGNMENT-6 HINTS & SOLUTIONS of Q8, Q9 & Q10

8. Design a self bias circuit using a Ge transistor with $V_{CC}=16V$ and $R_C=1.5K\Omega$ for obtaining of $V_{CE}=8V$ and $I_C=4mA$. Assume $S=12$ & $\beta=50$.


Design a self-bias circuit using Ge transistor with $V_{CC}=16V$, $R_C=1.5K\Omega$ for fixing the Q-point at $(4mA, 8V)$. Assume $S=12$ and $\beta=50$. (I_C, V_{CE})

The self-bias circuit is shown below:

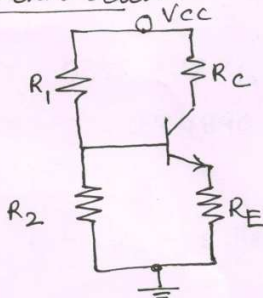


Ge Transistor
i.e, $V_{BE}=0.3V$
If Si-Transistor take $V_{BE}=0.7V$

The circuit with given data

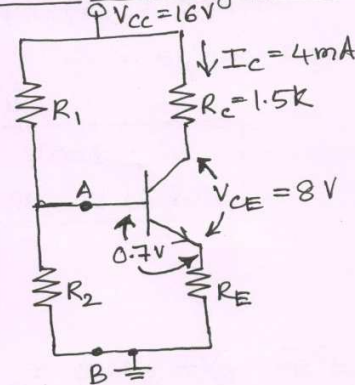

As part of the design so we need to calculate the values of R_1, R_2 and R_E

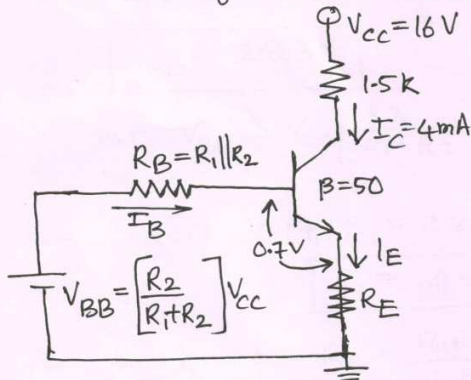Thevenin's equivalent circuit across points A & B.



$I_C = \beta I_B \Rightarrow I_B = \frac{I_C}{\beta}$

$I_B = \frac{4mA}{50} = 0.08mA$

$I_E = I_C + I_B = 4mA + 0.08mA$

$I_E = 4.08mA$

$V_{CC} = I_C R_C + V_{CE} + I_E R_E$
 $16 = (4mA)(1.5K) + 8V + (4.08mA) R_E$
 $16 = 6 + 8 + (4.08mA) R_E$
 $R_E = \frac{16 - 14}{4.08mA} = 0.490K\Omega$

(or) $R_E = 490\Omega$ ✓

✓ Use stability factor expression to get some values

$$S = \frac{1+\beta}{1+\beta \left[\frac{R_E}{R_E+R_B} \right]} \Rightarrow 12 = \frac{1+50}{1+50 \left[\frac{490\Omega}{490+R_B} \right]}$$

$$\Rightarrow 12 + 600 \left(\frac{490}{490+R_B} \right) = 51 \Rightarrow 12(490+R_B) + 294000 = 51(490+R_B)$$

$$\Rightarrow 5880 + 12R_B + 294000 = 24990 + 51R_B$$

$$\Rightarrow 274890 = 39R_B \Rightarrow R_B = 7048.46\Omega$$

(or) $7.05\text{ k}\Omega$

✓ But $R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$

✓ Write KVL to Input loop eqⁿ: $V_{BB} = I_B R_B + V_{BE} + I_E R_E$

$$\therefore V_{BB} = (0.08\text{mA})(7.05\text{k}\Omega) + 0.3 + (4.08\text{mA})(0.490\text{k}\Omega)$$

$$V_{BB} = 0.564 + 0.3 + 1.992 = 2.8632\text{V}$$

$$V_{BB} = 2.863\text{V}$$

✓ But $V_{BB} = V_{CC} \left[\frac{R_2}{R_1 + R_2} \right] = 16 \left[\frac{R_2}{R_1 + R_2} \right] \Rightarrow \frac{2.863}{16} = \frac{R_2}{R_1 + R_2}$

$$0.179 = \frac{R_2}{R_1 + R_2}$$

(or) $0.179R_1 = 0.821R_2$


$$R_1 = 4.587R_2$$

✓ we know $R_B = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow 7.05\text{ k} = \frac{(4.587R_2)R_2}{5.587R_2}$

(or) $R_2 = \frac{(7.05)(5.587)}{4.587} = 8.587\text{ k}\Omega$

As $R_1 = 4.587R_2 = (4.587)(8.587\text{ k}\Omega) = 39.389\text{ k}\Omega$

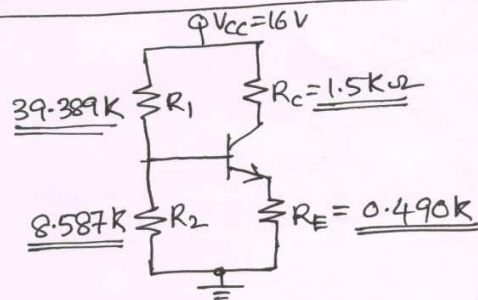Hence the circuit with the designed values is




9.


For a fixed bias circuit using Ge-transistor with $R_B = 100\text{k}\Omega$, $R_C = 22\text{k}\Omega$, $V_{CE} = 4\text{V}$, $V_{CC} = 10\text{V}$, find the stability factor.

Sol:

The fixed bias circuit is shown below

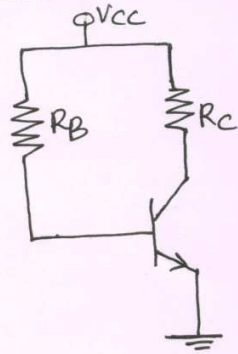

The circuit with given data

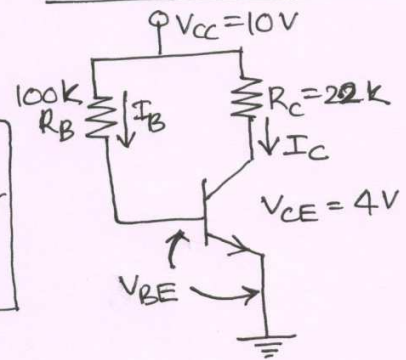

Given
Ge-transistor
So $V_{BE} = 0.3\text{V}$

✓ The stability factor of fixed bias circuit is $(1 + \beta)$

So we need to calculate, first, β of the transistor,

→ β can be estimated from I_C and I_B values, as $\beta = \frac{I_C}{I_B}$

✓ KVL to input loop: $V_{CC} = I_B R_B + V_{BE} \Rightarrow 10 = I_B (100\text{k}) + 0.3$

$$I_B = \frac{10 - 0.3}{100\text{k}} = 0.097\text{mA} \quad (\text{or}) \quad \boxed{I_B = 0.097\text{mA}}$$

✓ KVL to output loop: $V_{CC} = I_C R_C + V_{CE} \Rightarrow 10 = I_C (22\text{k}) + 4$

$$I_C = \frac{10 - 4}{22\text{k}} = 0.273\text{mA} \quad (\text{or}) \quad \boxed{I_C = 0.273\text{mA}}$$

✓ β -of the transistor: $\beta = \frac{I_C}{I_B} = \frac{0.273\text{mA}}{0.097\text{mA}} = 2.82$

✓ stability factor $S = 1 + \beta \Rightarrow S = 1 + 2.82 \Rightarrow \boxed{S = 3.82}$

✓ $S = 3.82$

$$\frac{dI_C}{dI_{E0}} = 3.82 \Rightarrow dI_C = (3.82)dI_{E0}$$


i.e., the collector current changes by 3.82 times as much as the reverse leakage current (I_{E0}) changes //.

10.

Q-10 | A6 | 2015-16 | II sem


Design a collector to base bias circuit with $V_{CC} = 15V$, $V_{CE} = 5V$, $I_C = 5mA$, $\beta = 100$.

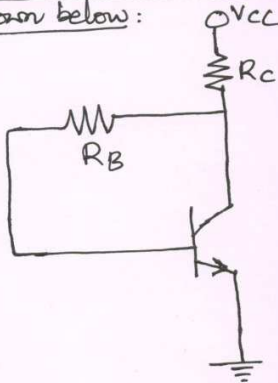d: The collector to base bias circuit is shown below:



As transistor type is not mentioned. let us assume Si-transistor
 $\therefore V_{BE} = 0.7V$

The circuit with given data

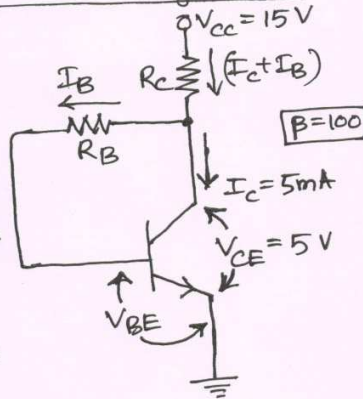

$I_C = \beta I_B \Rightarrow I_B = \frac{I_C}{\beta} = \frac{5mA}{100} = 0.05mA$

$I_B = 0.05mA$

As part of design, we need to calculate the values of R_C & R_B

✓ KVL to output loop:

$V_{CC} = R_C(I_C + I_B) + V_{CE} \Rightarrow 15 = R_C(5mA + 0.05mA) + 5$

$\Rightarrow R_C = \frac{15-5}{5.05mA} = 1.980k\Omega$ (or) $R_C = 1.980k\Omega$


✓ To find R_B : Instead of writing input loop eqⁿ, we use simple transistor voltage relationship

$V_{CE} = V_{CB} + V_{BE}$

$5 = I_B R_B + 0.7$

$R_B = \frac{5-0.7}{I_B} = \frac{4.3}{0.05mA} = 86k\Omega$

$R_B = 86k\Omega$

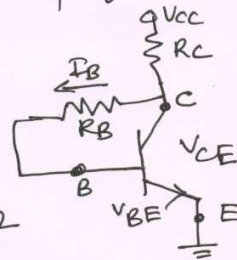

\therefore The circuit with the designed values is shown here

*** Stability factor of this ckt ***
 $S = \frac{1+\beta}{1+\beta(\frac{R_C}{R_C+R_B})}$
 $= \frac{1+100}{1+100(\frac{1.98}{1.98+86})}$
 $S = 31$

Remember \rightarrow